Name : _____ Physics 4B/Exam 2 Winter 2003

Two concentric spherical conducting shells are separated by vacuum. The inner shell has total charge +Q and outer radius 'a' and the outer shell has charge -Q and inner radius 'b' a) Find the capacitance of this spherical capacitor. (5 pts)



b) If the region between the spherical shells is filled with silicon with resistivity $\rho = 2300 \ \Omega \ m$, find the resistance between the shells assuming a = 10cm and b = 30 cm. (5 pts)

- 2. The figure below shows the voltage across a capacitor that is charging through a 4700 Ω resistor. Use the graph to determine: (10 pts)
 - a) The battery voltage.
 - b) The time constant.
 - c) The capacitance of the capacitor.
 - d) The maximum charge on capacitor.



- 3. In the circuit below the switch is initially open and both capacitors initially uncharged. All resistors hace the same value R. (10 pts)
 - a) Find the current through R_2 just after the switch is closed.
 - b) Find the current through R_2 a long time after the switch has been closed.
 - c) **DESCRIBE QUALITATIVELY** how you expect the current in R_3 to behave after the switch is closed.
 - d) Draw a sketch of the graph of I_3 vs. t for the current through R_3 after the switch has been closed until a long time after it has been closed.



- 4. Consider the circuit below. (10 pts)
 - a) What is the total number of currents in the circuit?
 - b) Write down the required equations to solve for all the current in the cirucit.
 - c) Assuming the current from 'a' to 'b' is + 0.385mA, find the currents in the rest of the circuit.
 - d) Find the potential of point 'c' relative to point 'e'. Which point is at a higher potential?

